

0.5 Solution

Truth Table

P	Q	R	S	H
0	0	0	0	1
0	0	0	1	1
0	0	1	0	1
0	0	1	1	1
0	1	0	0	0
0	1	0	1	1
0	1	1	0	0
0	1	1	1	1
1	0	0	0	1
1	0	0	1	1
1	0	1	0	1
1	0	1	1	0
1	1	0	0	0
1	1	0	1	0
1	1	1	0	1
1	1	1	1	1

Table 5.0

1.The following K-map is obtained from the above truth table.

2.As we have Four Variables we obtain a 16 cell K-Map

PQ	RS			
	00	01	11	10
00	1	1	1	1
01	0	1	1	0
11	0	0	1	1
10	1	1	0	1

Table 5.1

3.Now we do grouping to obtain the minimal expression using the K-Map.

PQ	RS			
	00	01	11	10
00	1	1	1	1
01	0	1	1	0
11	0	0	1	1
10	1	1	0	1

Table 5.2

The minterm expression for the two groupings are $\overline{Q}S$ and $\overline{P}S$

PQ	RS			
	00	01	11	10
00	1	1	1	1
01	0	1	1	0
11	0	0	1	1
10	1	1	0	1

Table 5.3

The minterm expression for the two groupings are PQR and $P\overline{Q}R$

PQ	RS			
	00	01	11	10
00	1	1	1	1
01	0	1	1	0
11	0	0	1	1
10	1	1	0	1

Table 5.4

The Minimal expression is

$$H = \overline{Q}S + \overline{P}S + PQR + P\overline{Q}R$$

4.Download the code from the given link and upload to the Arduino.

<https://github.com/siva-gayathri/FWC/blob/main/assignment-1/codes/src/main.cpp>

5.Go to the working directory execute pio run and pio run -t upload.

6.Whenever you change the inputs you will see the respective output.